

Mechatronics (ROB-GY 5103 Section A)

- **Today's lecture:**
 - Multivibrator (555 timer)
- (See Topics #4 from Main Text for details)

Review of RC Circuit


- What is the time constant?
- Why does 63.2% mean?

Two-state devices

- Button/switch provides digital (two-state) inputs
- Comparator produces digital output
- Deceptively simple:
 - Pull-up/pull-down and active-high/active/low
 - Use hysteresis to remove chattering in a comparator


Two-state devices

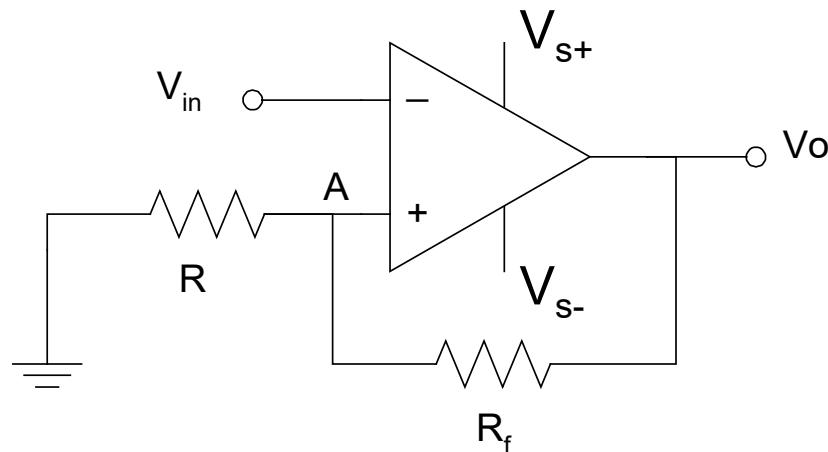- Button/switch provides digital (two-state) inputs
- Comparator produces digital output
- Deceptively simple:
 - Pull-up/pull-down and active-high/active/low
 - Use hysteresis to remove chattering in a comparator




SR Latch (Set-Reset Latch)

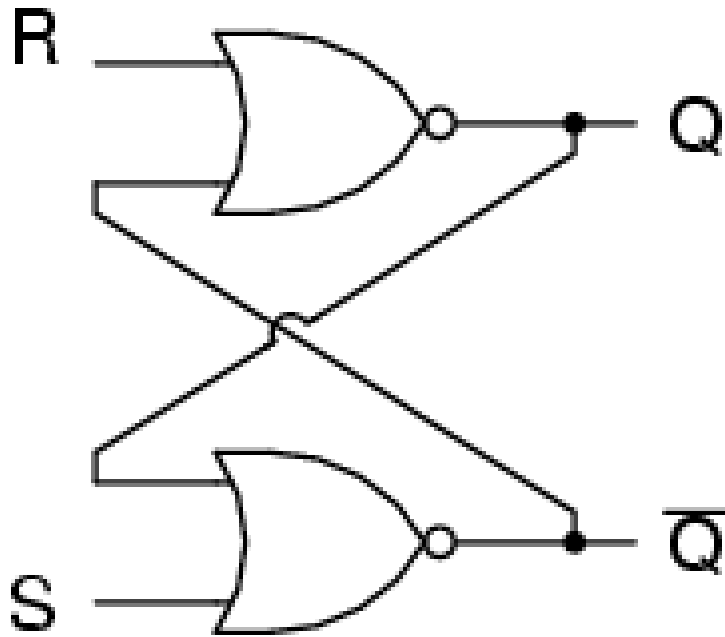- Simple **active** two-state device with two NOR gates



SR Latch (Set-Reset Latch)

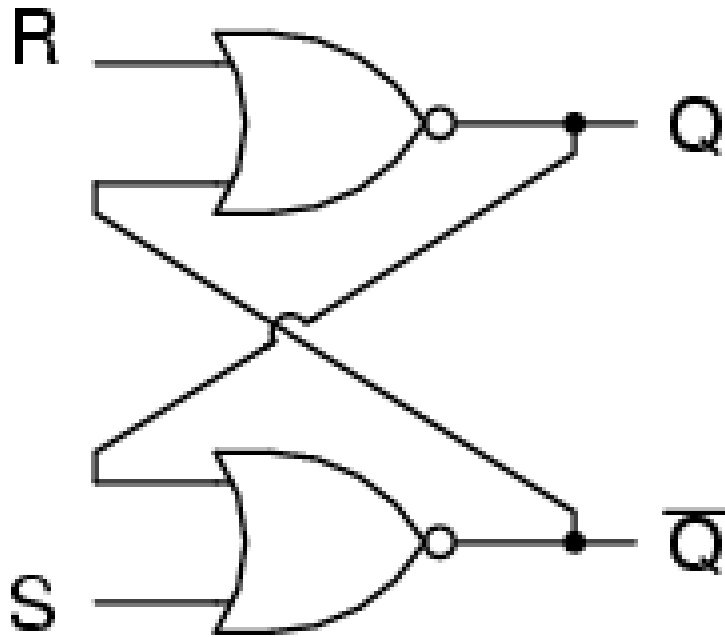
- Simple **active** two-state device with two NOR gates



S	R	Q	\bar{Q}
0	0	latch	latch
0	1	0	1
1	0	1	0
1	1	0	0

SR Latch (Set-Reset Latch)

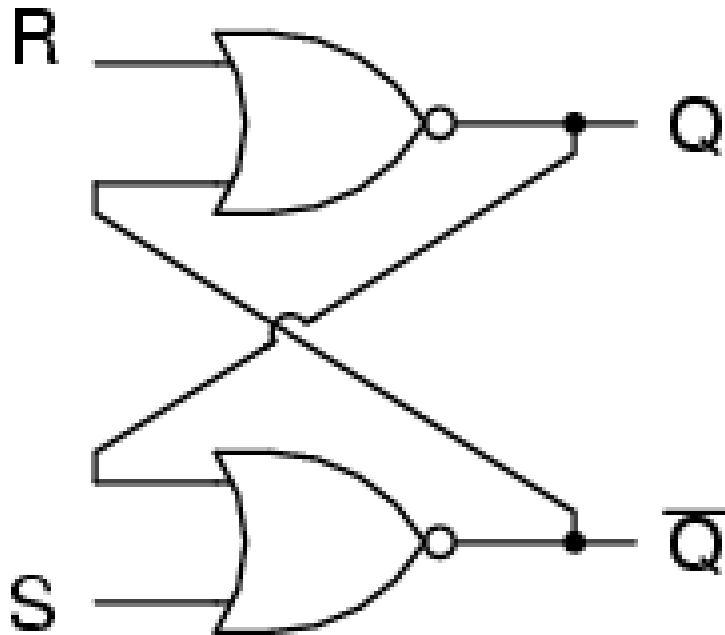- Simple **active** two-state device with two NOR gates
- System has memory!




S	R	Q	\bar{Q}
0	0	latch	latch
0	1	0	1
1	0	1	0
1	1	0	0

Multivibrator

- **Astable** multivibrator circuit
 - Oscillates between two states
 - No trigger input
- **Monostable** multivibrator circuit (**one-shot** circuit)
 - Stable in one state (transient in the other state)
 - One trigger input
- **Bistable** multivibrator circuit
 - Stable in either state
 - Two trigger inputs (on/off) or toggle
 - Building block for memory

555 timer

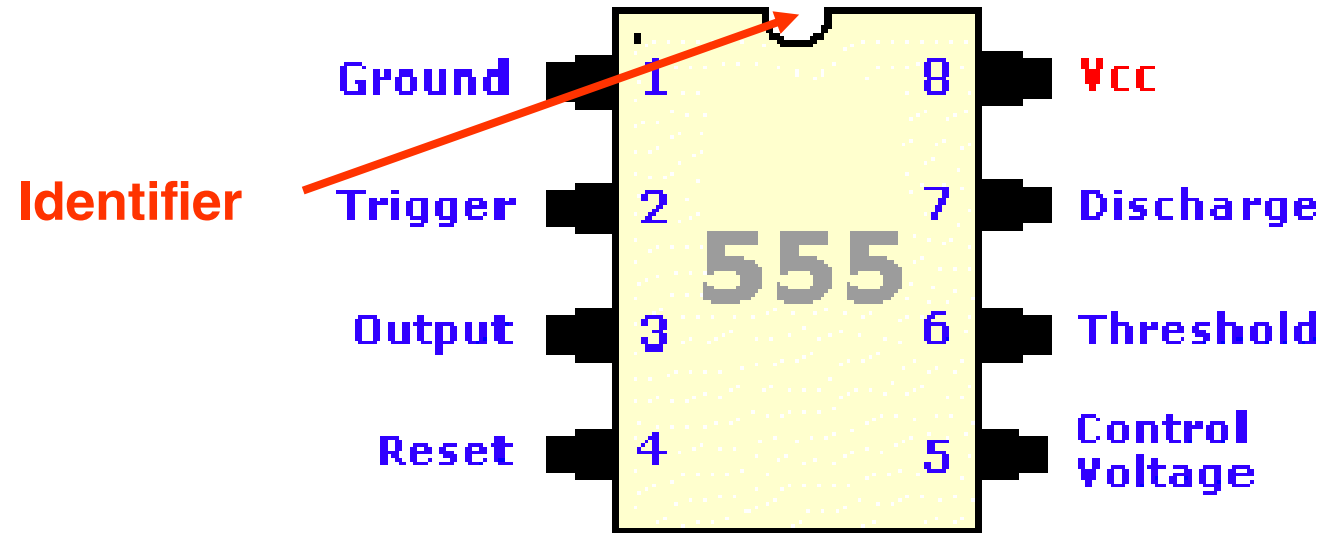
- Highly stable device for generating accurate time delay or oscillation.
- Not programmable.
 - Controlled by resistors and capacitors.
- Applications
 - Pulse generation
 - PWM
 - Time delay generation




Pinout Diagram

555 Timer: Block Diagram

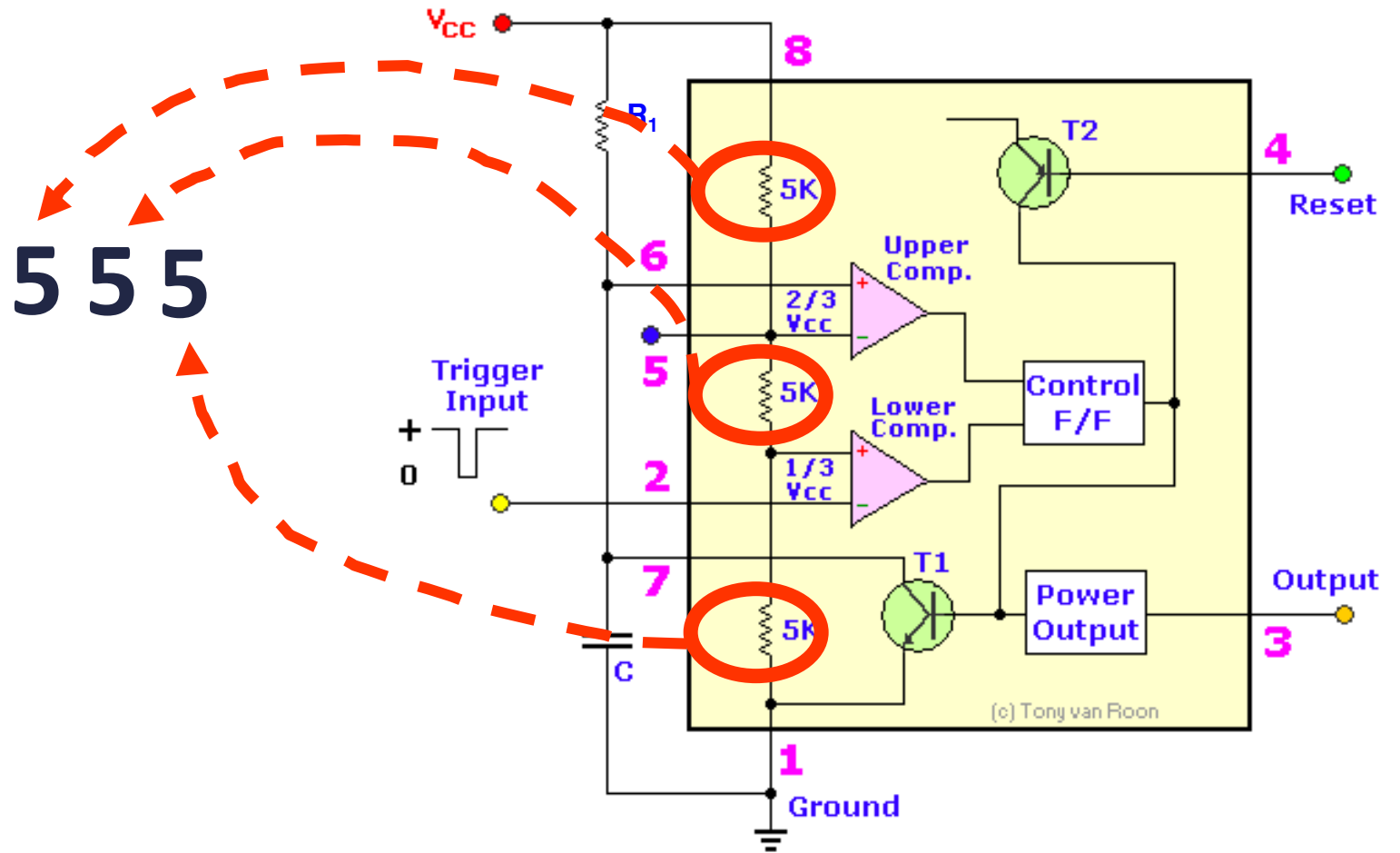- Contains **control flip-flop**
 - Same truth table as **SR Latch**
- Voltage divider formed by three 5K ohm resistors
- Two comparators
- Two transistors



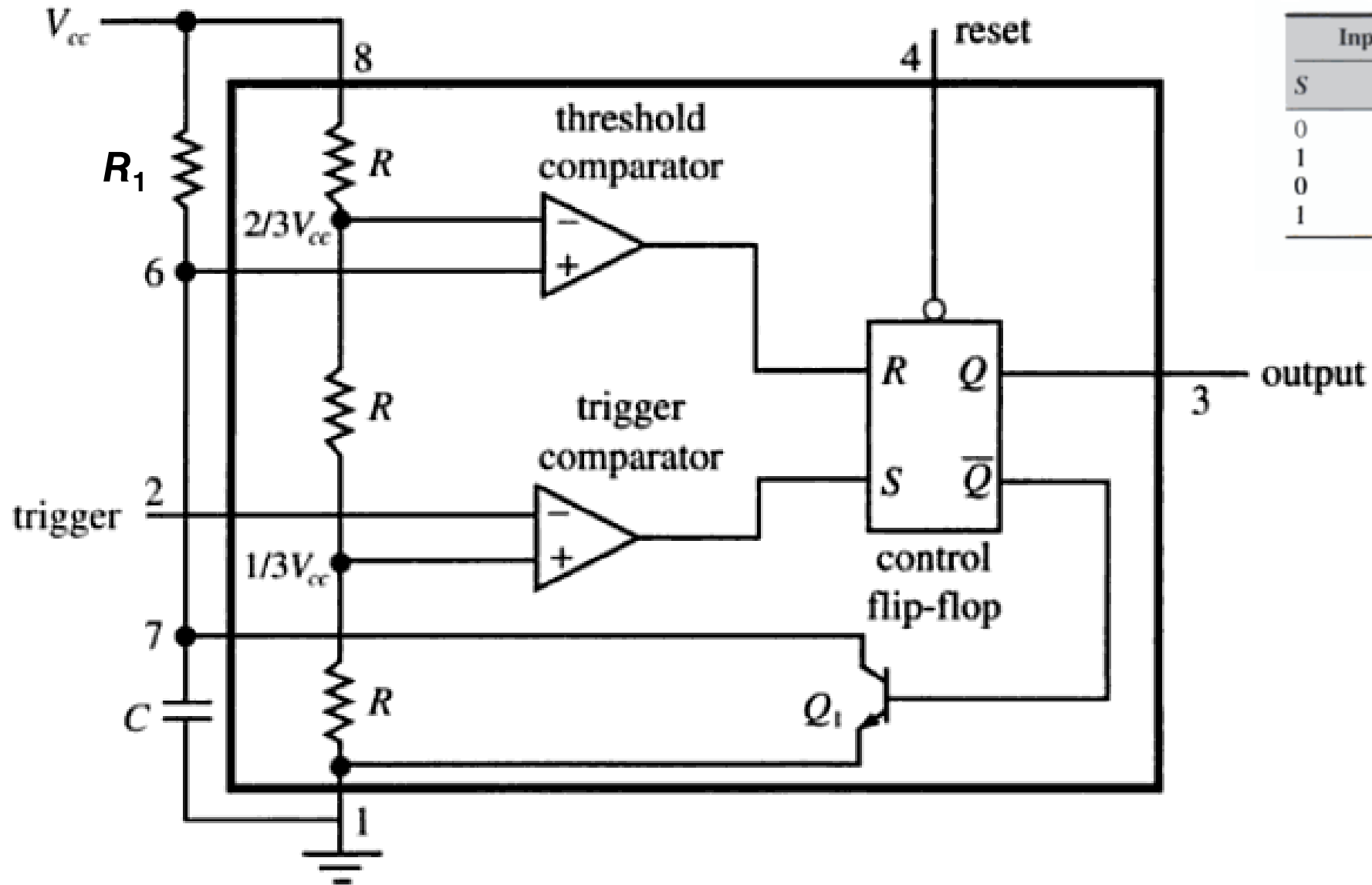
555 Timer: Monostable Mode Implementation



Truth table for the RS flip-flop


Inputs		Outputs	
S	R	Q	\bar{Q}
0	0	Q_0	\bar{Q}_0
1	0	1	0
0	1	0	1
1	1	NA	

555 Timer: Monostable Mode Output

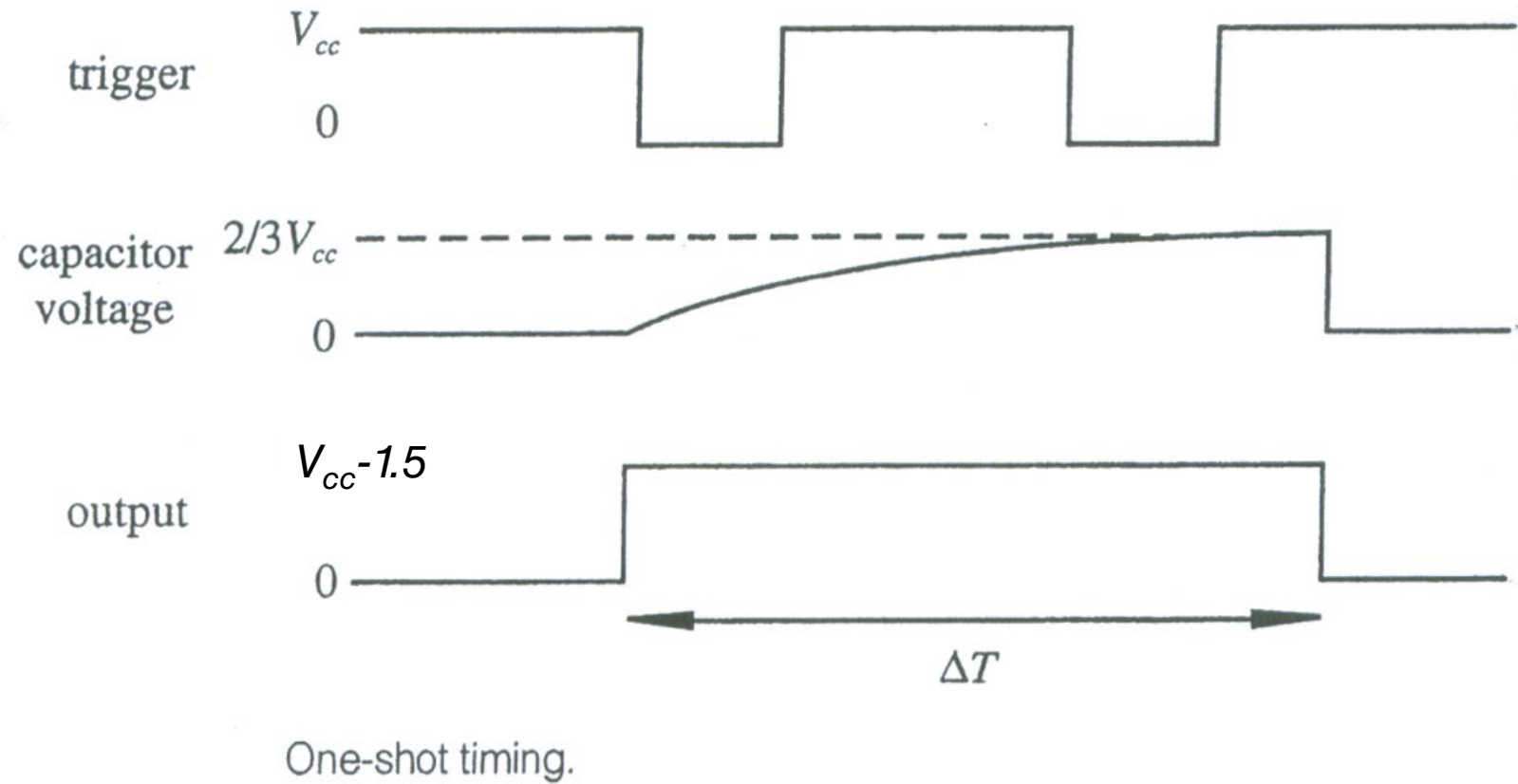

555 Timer: Monostable Circuit Operation

- On power-up or after reset: $Q = \text{low} \rightarrow \text{output low}, \bar{Q} = \text{high} \rightarrow$ transistor Q_1 in saturation \rightarrow capacitor C is shorted
 - Threshold comparator: $V_- = (2/3)V_{cc}$ and $V_+ = 0 \rightarrow$ comparator o/p low ($R=0$)
 - Trigger comparator: $V_- = \text{High}$ and $V_+ = (1/3)V_{cc} \rightarrow$ comparator o/p low ($S=0$)
 - $R=0, S=0 \rightarrow Q$ and \bar{Q} maintain their initial state

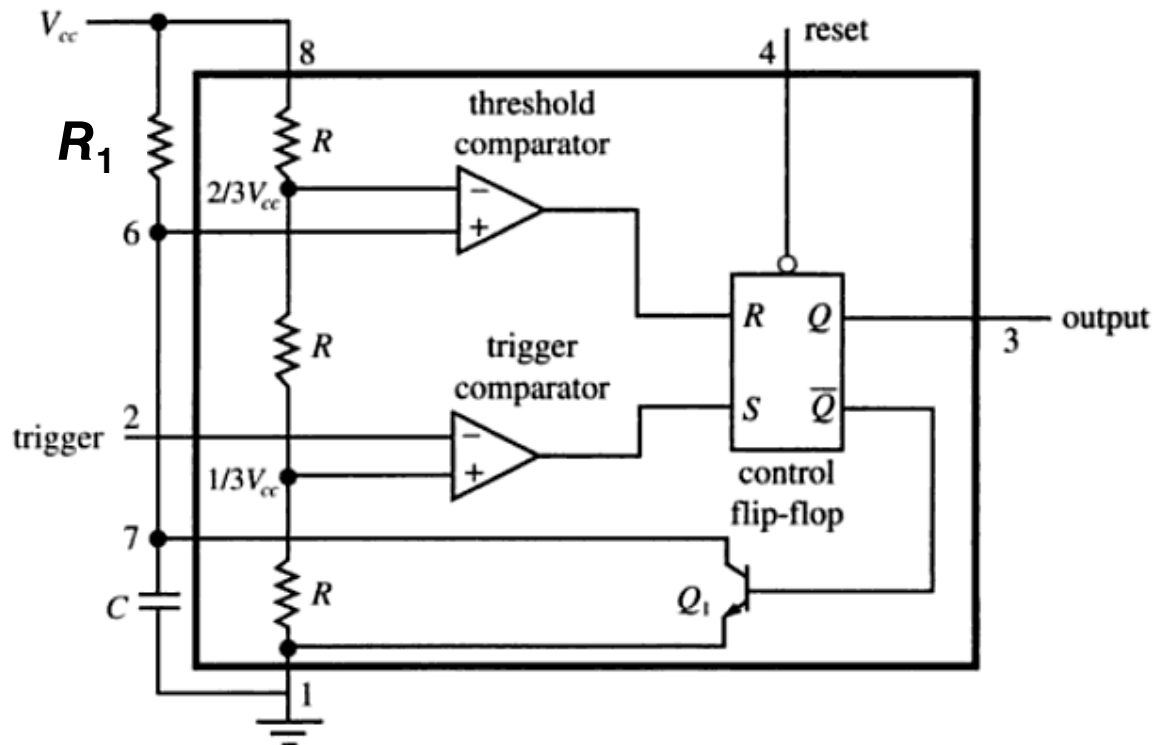

Truth table for the RS flip-flop

Inputs		Outputs	
S	R	Q	\bar{Q}
0	0	Q_0	\bar{Q}_0
1	0	1	0
0	1	0	1
1	1	NA	

- S: set i/p
- R: reset i/p
- Q, \bar{Q} complementary o/ps

555 Timer: Monostable Circuit Operation

- When trigger pulse goes low (below $(1/3)V_{cc}$), momentarily,
 - o Trigger comparator: $V_- = \text{low}$ and $V_+ = (1/3)V_{cc} \rightarrow$ comparator o/p high ($S=1$)
 - o Threshold comparator: $V_- = (2/3)V_{cc}$ and $V_+ = \text{voltage across capacitor}$ which charges from 0V initial state towards $(2/3)V_{cc} \rightarrow$ comparator o/p low ($R=0$)
 - o $R=0, S=1 \rightarrow Q = 1$ (output high) and $\bar{Q} = 0$ transistor stops conducting
 - o This state persists until threshold comparator: $V_+ = (2/3)V_{cc}$ then $R=1$ and $S=0$ (since trigger goes low only momentarily) $\rightarrow Q=0$ (output low) and $\bar{Q}=1$ so transistor conducts again and causes the capacitor to be shorted.
 - o Note that the capacitor charges from 0V initial state towards $(2/3)V_{cc}$ with time constant R_1C


555 Timer: Monostable Circuit Operation

- This circuit has only one stable state.
- The o/p resets at 0V, until a negative-going trigger pulse is applied to the trigger lead: pin 2.
- After trigger pulse is applied, the o/p will go high (around $V_{cc}-1.5V$) for the duration set by R_1C network.

- The width of the high output pulse is:
$$t_{width} = 1.10R_1C$$
$$V_c(t) = V_{cc}(1 - e^{-t/\tau})|_{t=1.1\tau}$$
$$V_c(1.1\tau) = \frac{2}{3}V_{cc}$$


- For reliable operation, R_1 should be between 10kW and 14MW and the capacitor should be from around 100pF to 1000mF.

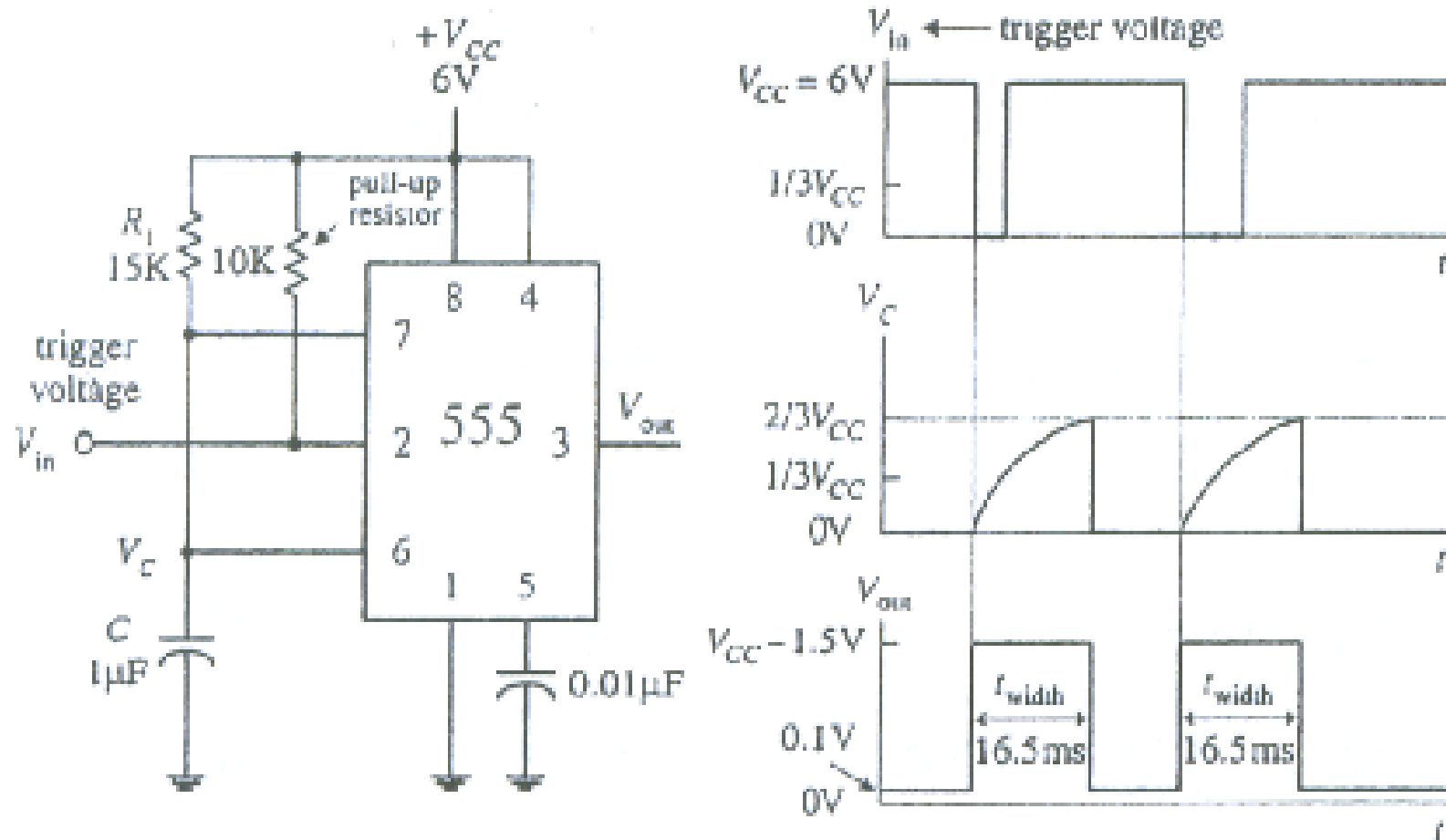555 Timer: Monostable Circuit Operation—IV



$$t_{width} = 1.10 R_1 C$$
$$t_{width} = 1.10 (15K)(1\mu F) = 16.5ms$$

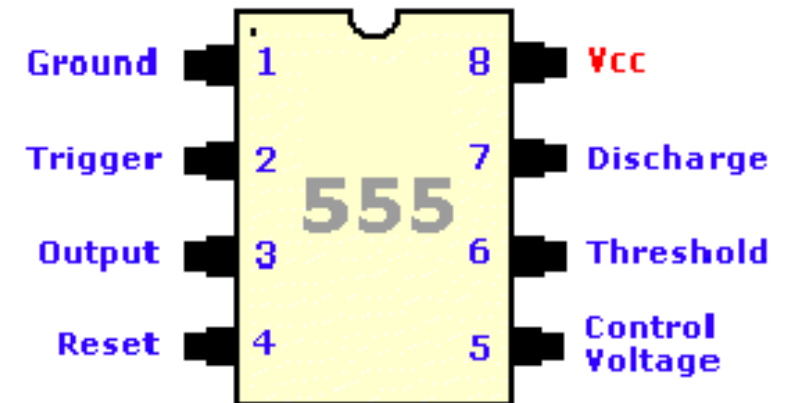- Note capacitor at pin 5
 - Buffer to stabilize voltage at the pin
- In general, pin 5 is used to override voltage of $2/3 V_{CC}$




555 Timer: Monostable Mode Application: Delay Timer for Relay

- Delay timer to actuate a relay for a given duration
- When the push-button is momentarily closed, the 555 begins its timing cycle; the output goes high (in this case, ~10.5V) for a duration of


$$t_{width} = 1.10R_1C$$

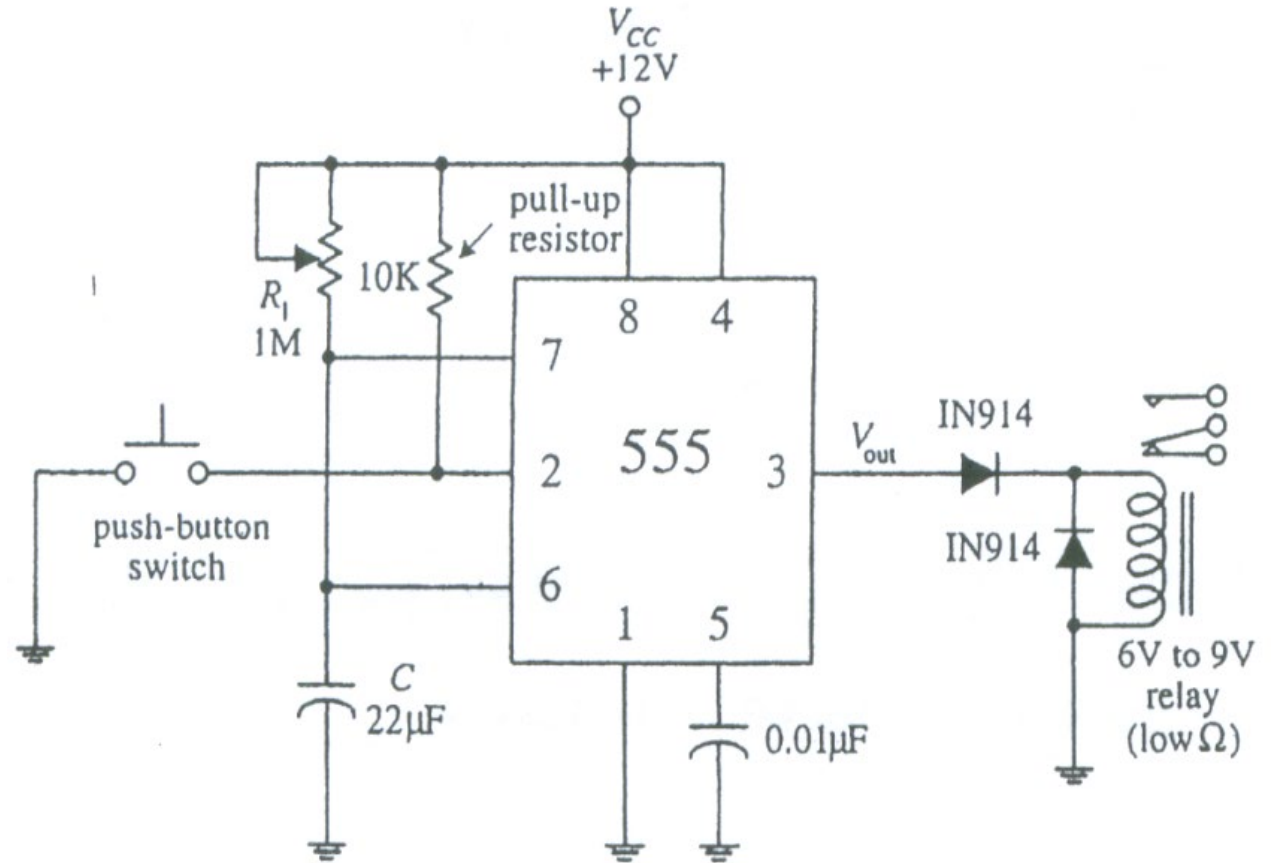- The relay is actuated for the same time duration.
- Diodes prevent inductive kickback from damaging the 555 IC and the switch contacts of relay




Recall: Switch Bounce

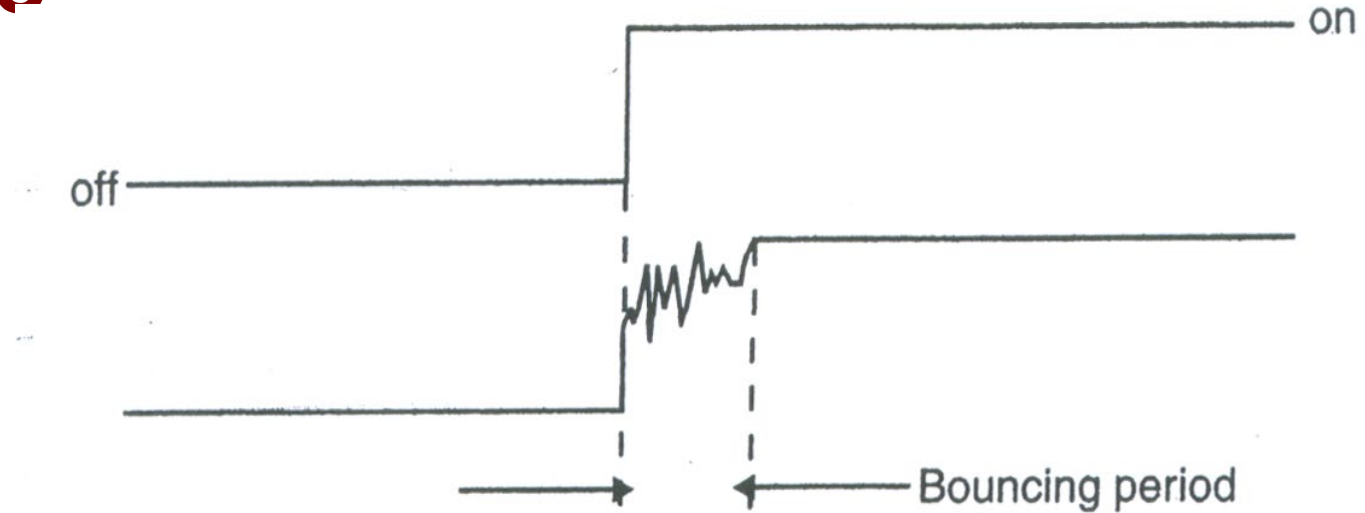- Mechanical switches often suffer from switch bounce.
 - switch chatters with multiple low-high transitions
- **Debouncing** removes bounce
 - **Hardware:** RC circuit can be used
 - **Code:** BS2 command “Button” can be used to eliminate switch bounce in software (needs 250 μ sec)



Contact bounce when turning on a switch.

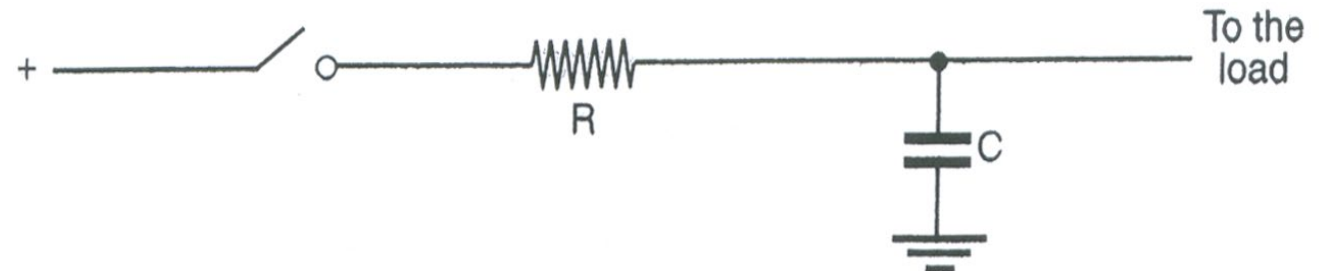

Simple debouncing.


This circuit may cause time delay.

Another Hardware Solution for Debouncing


- **Monostable** circuit (**one-shot** circuit)
 - Function is to produce a single output pulse which goes from low to high and back to low once the switch is pressed
 - If a switch closing happens too quickly for BS2 to register, then the monostable circuit can be quite useful
 - Duration for high pulse output is controlled by appropriate selection of R and C
 - not useful for monitoring the current state in real time

555 Timer: Monostable Mode Application: Debouncing

- Uses a **555 timer**

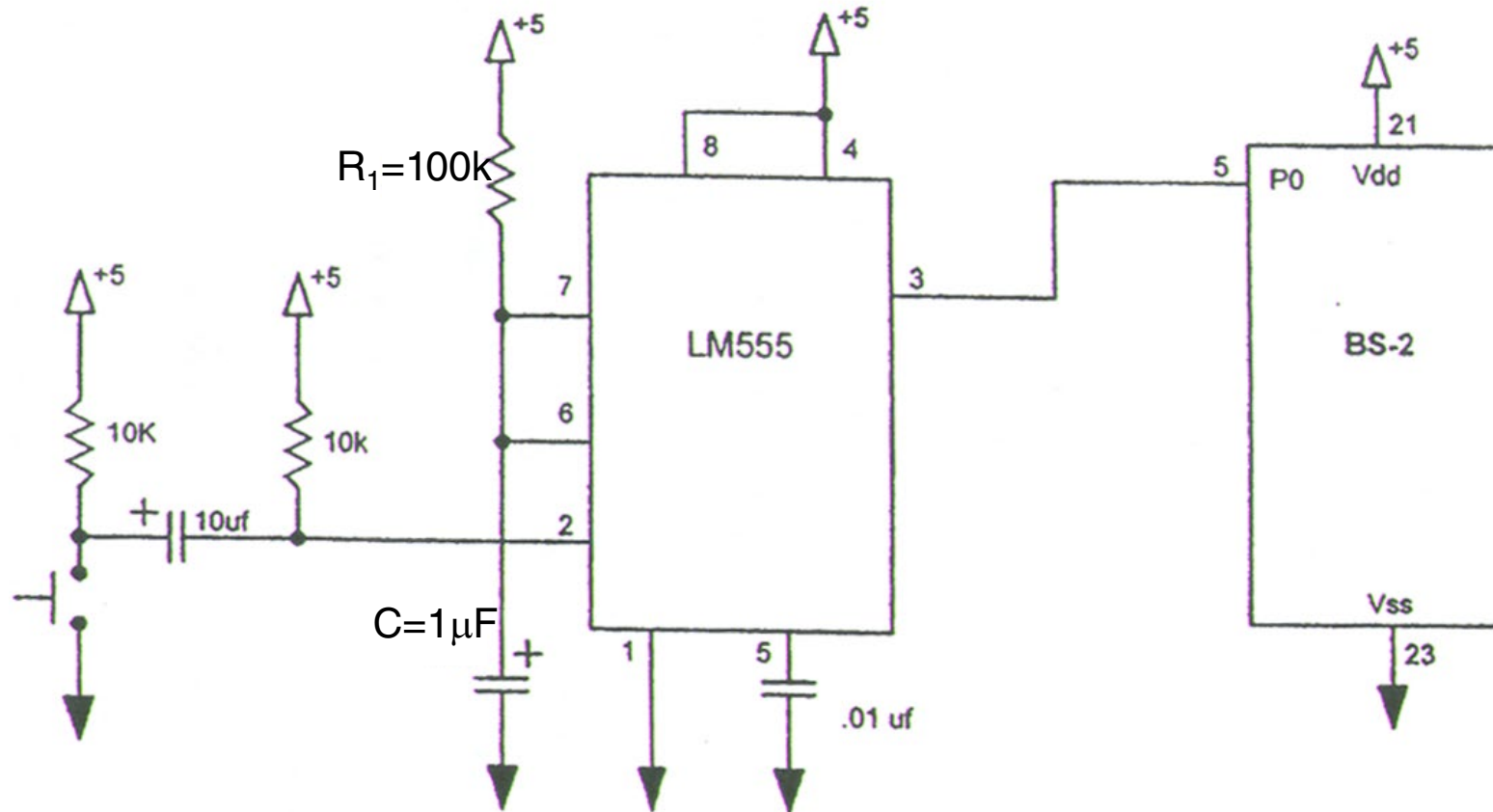


555 Timer: Astable Mode

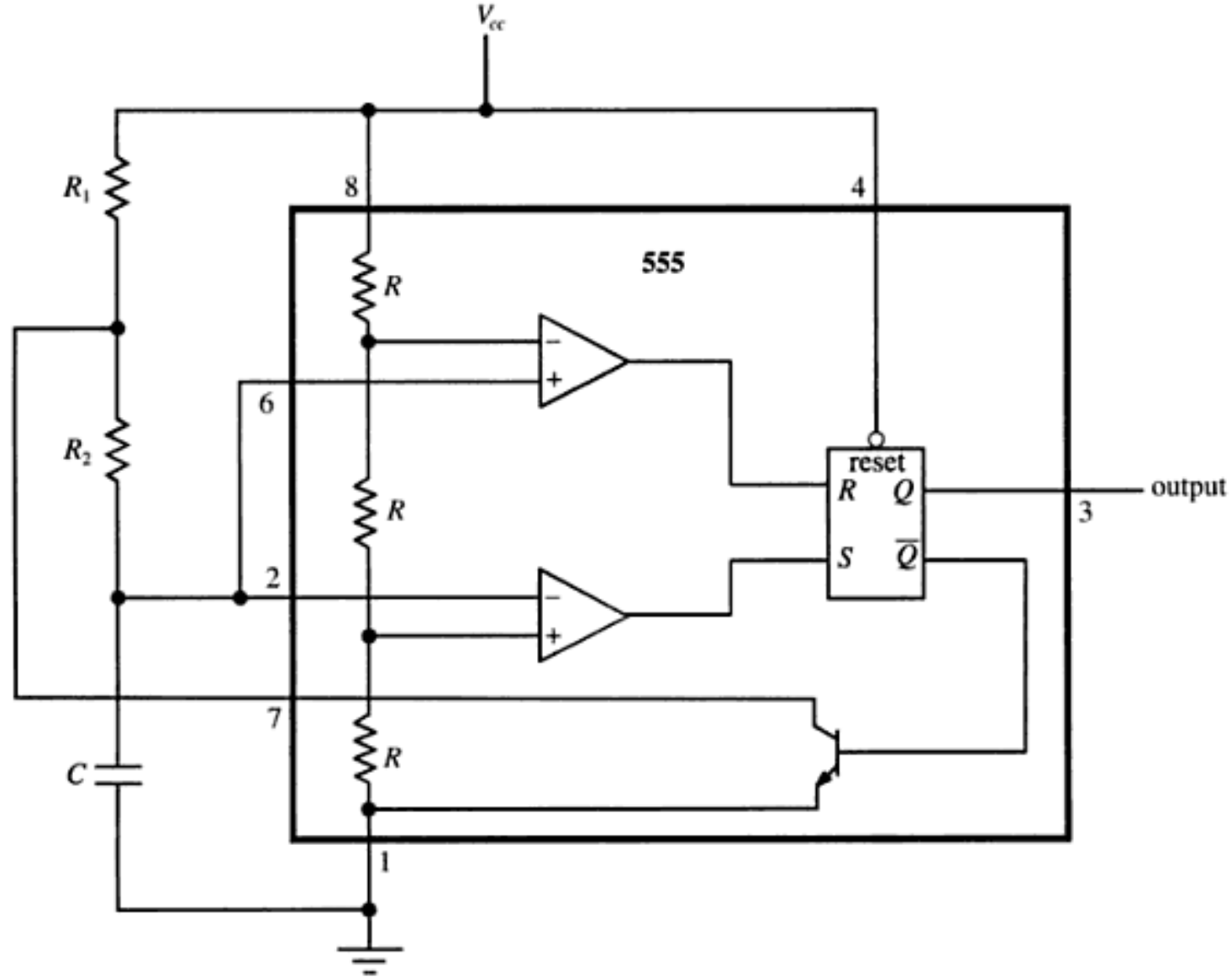

555 Timer: Astable Mode Operation


- On power-up: C is discharged, so pin 2 is low (0V), Comp2: $V_- = 0$, $V_+ = (1/3)V_{cc} \rightarrow S=1$, Comp1: $V_+ = 0$, $V_- = (2/3)V_{cc} \rightarrow R=0$, So $\rightarrow Q = 1$ and $\bar{Q} = 0 \rightarrow$ output is high, transistor not conducting, capacitor C charges via $R_1 + R_2$
 - Capacitor gets to $(1/3)V_{cc}$, Comp2: $V_- = (1/3)V_{cc}$, $V_+ = (1/3)V_{cc} \rightarrow S=0$, Comp1: $V_+ = (1/3)V_{cc}$, $V_- = (2/3)V_{cc} \rightarrow R=0$, So $\rightarrow Q$ and \bar{Q} do not change, output is high, transistor not conducting, capacitor C charges via $R_1 + R_2$
 - Capacitor gets to $(2/3)V_{cc}$, Comp2: $V_- = (2/3)V_{cc}$, $V_+ = (1/3)V_{cc} \rightarrow S=0$, Comp1: $V_+ = (2/3)V_{cc}$, $V_- = (2/3)V_{cc} \rightarrow R=1$, So $\rightarrow Q = 0$ and $\bar{Q} = 1 \rightarrow$ output is low, transistor conducts, capacitor C discharges via R_2

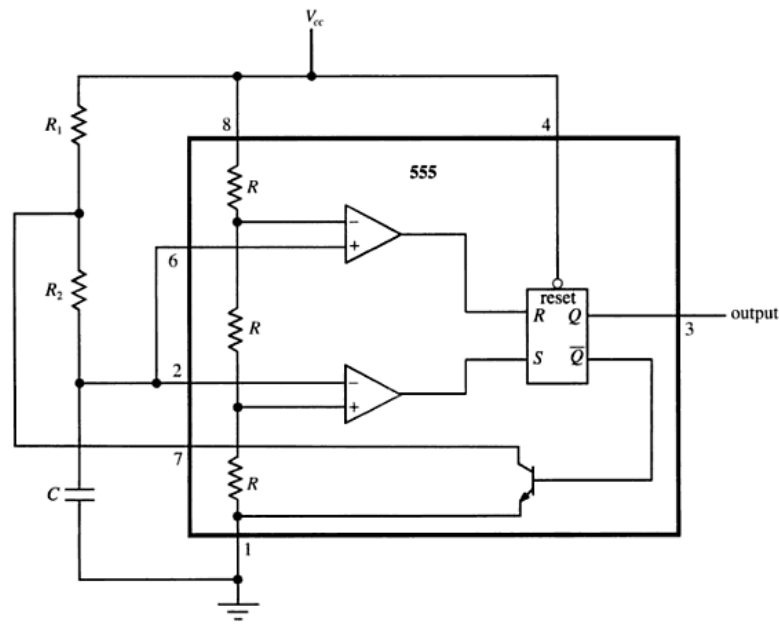


Truth table for the RS flip-flop

Inputs		Outputs	
S	R	Q	\bar{Q}
0	0	Q_0	\bar{Q}_0
1	0	1	0
0	1	0	1
1	1	NA	

555 Timer: Astable Mode Output

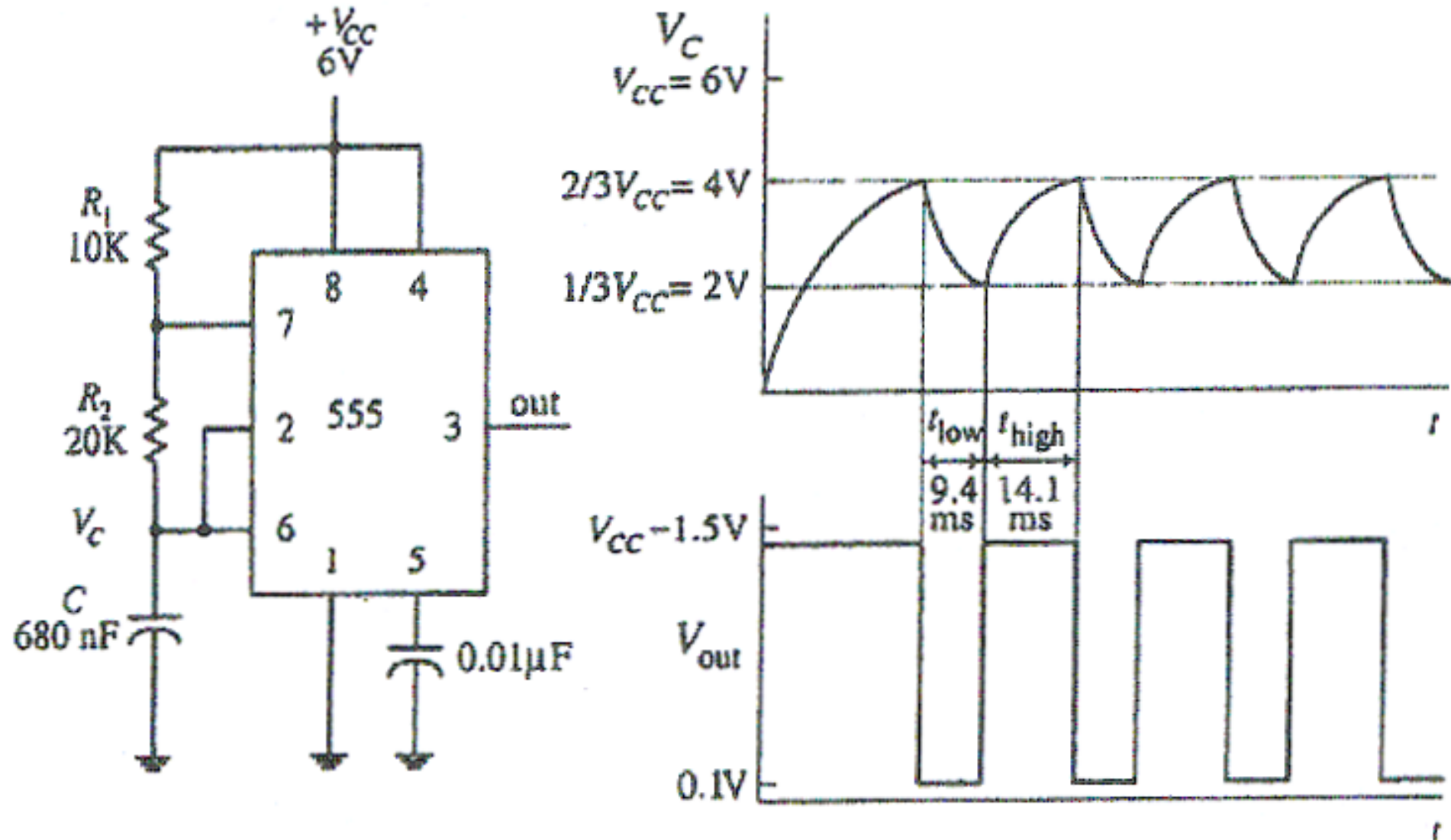

555 Timer: Astable Mode Duty Cycle

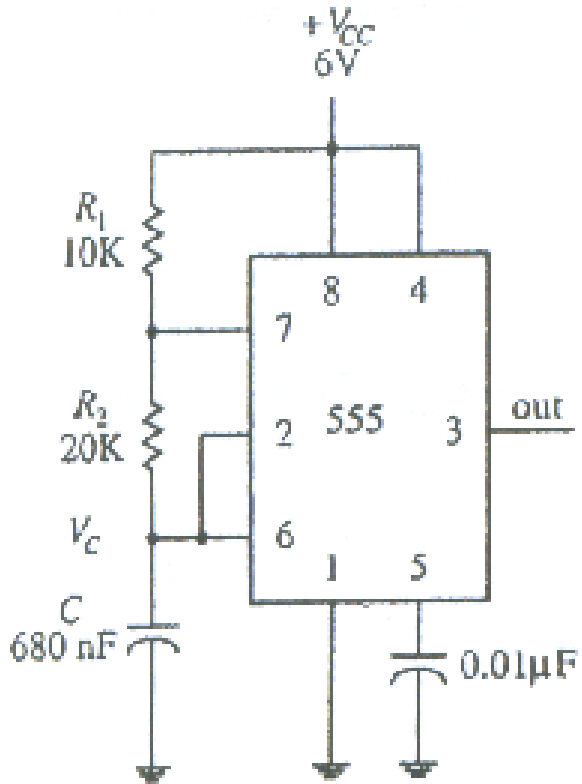


$$t_{low} = 0.693 R_2 C$$


$$t_{high} = 0.693 (R_1 + R_2) C$$

$$\text{Duty cycle} = \frac{t_{high}}{t_{high} + t_{low}}$$

$$f = \frac{1}{t_{high} + t_{low}}$$

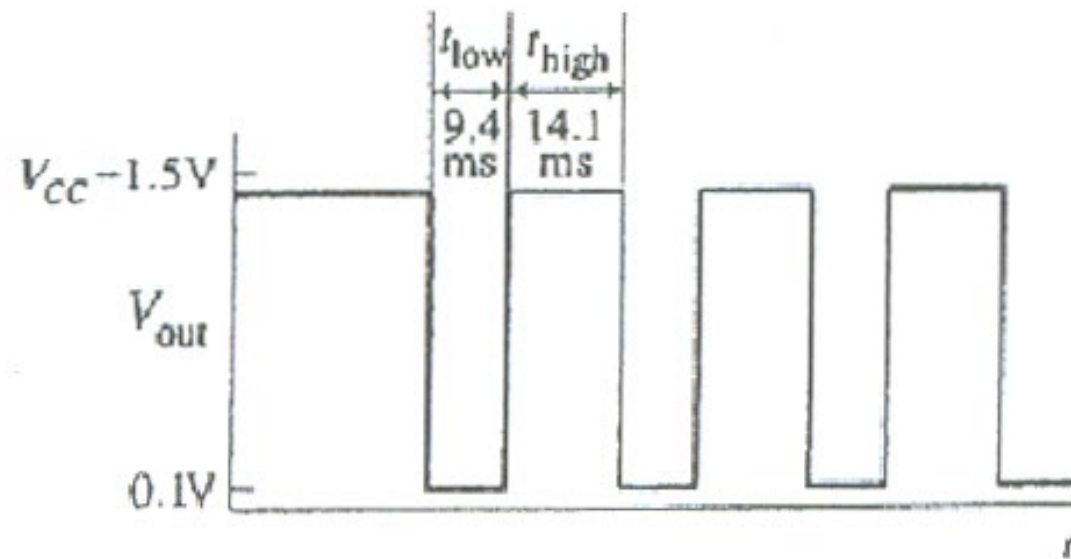

555 Timer: Astable Mode Duty Cycle

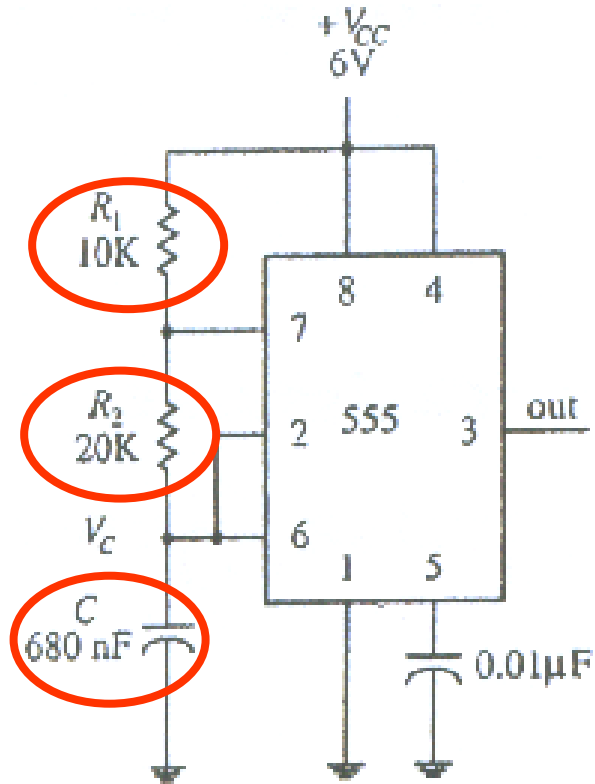


$$t_{low} = 0.693 (20K) (680nF) = 9.6ms$$

$$t_{high} = 0.693 (10K + 20K) (680nF) = 14.1ms$$

$$Duty\ cycle = \frac{14.1ms}{14.1ms + 9.6ms} = 0.6$$

$$f = \frac{1}{14.1ms + 9.6ms} = 42Hz$$

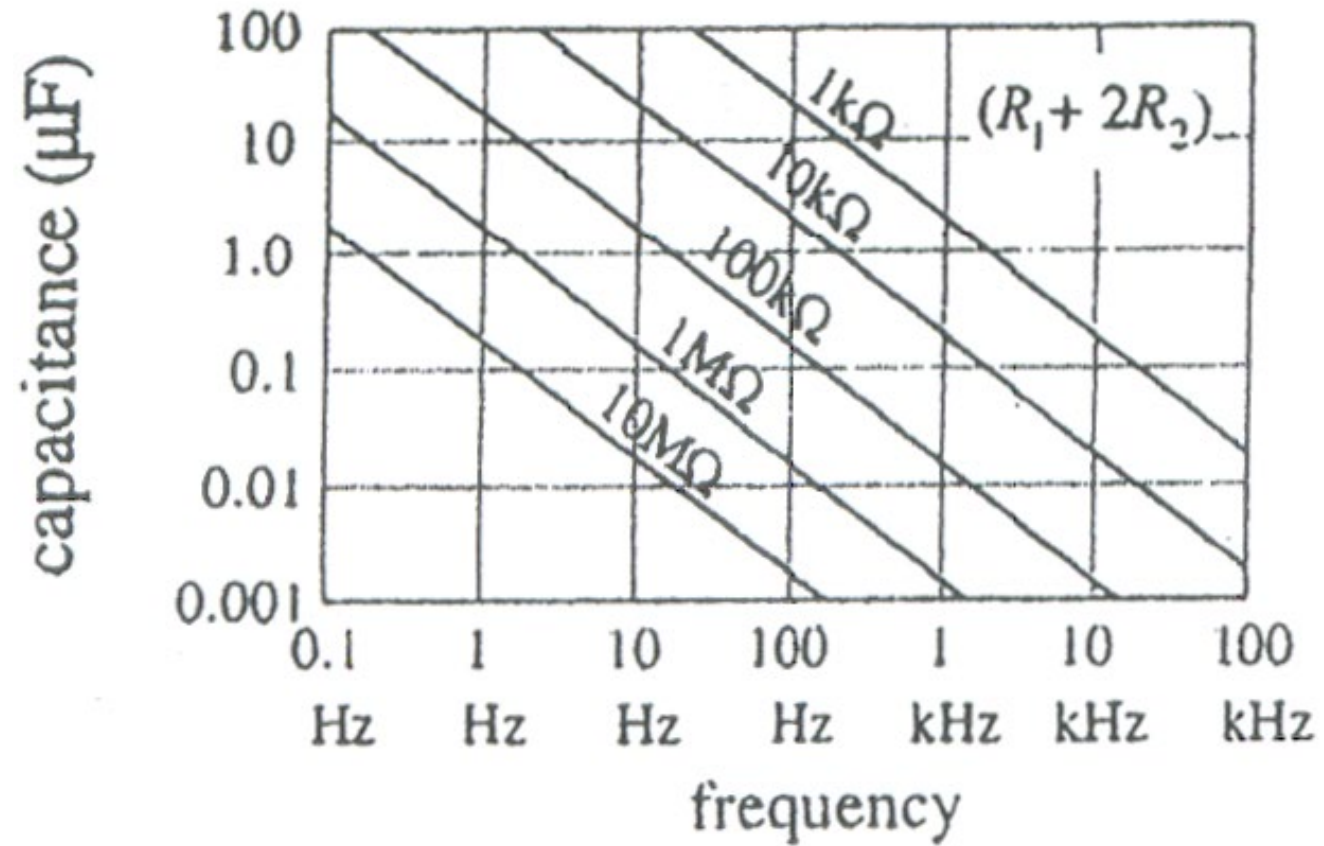555 Timer: Astable Mode Frequency vs. C, R_1 , and R_2



Measuring an Analog Value using Astable LM555 Timer

- The astable LM555 timer and the pulsin command of BS2 can be employed to measure the linear travel of a machine tool slide
- A pot is mechanically coupled to the arm undergoing linear motion via a rubber wheel.
- The translation motion of the arm changes the pot resistance.
- The pot resistance forms the “R1” resistor of the astable LM555 timer.
- Time duration of high pulse by 555 timer \propto Pot resistance \propto Linear travel of slide.

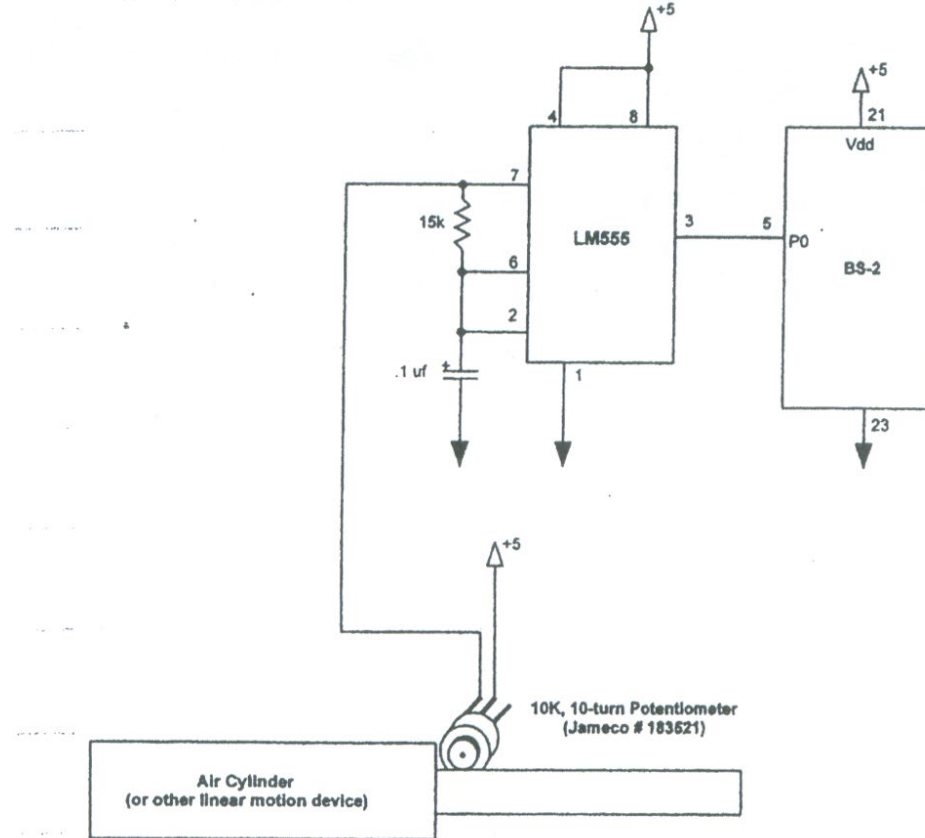



Figure
Using pulse-width modulation for linear movement detection

Pulsin 0, 1, Highdura

Will give time over which 555 outputs “high” pulse.


Simple Multivibrator

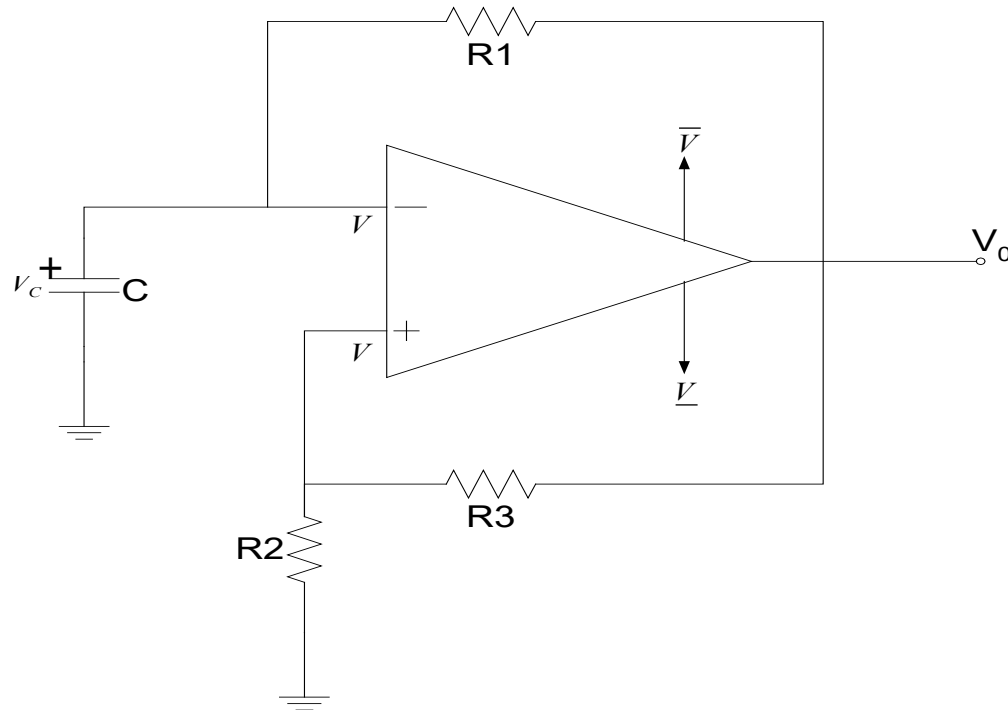- Consider a comparator with the given schematic.
 - Both positive and negative feedback
 - RC circuit that generates the inverting input V_- .




Simple Multivibrator

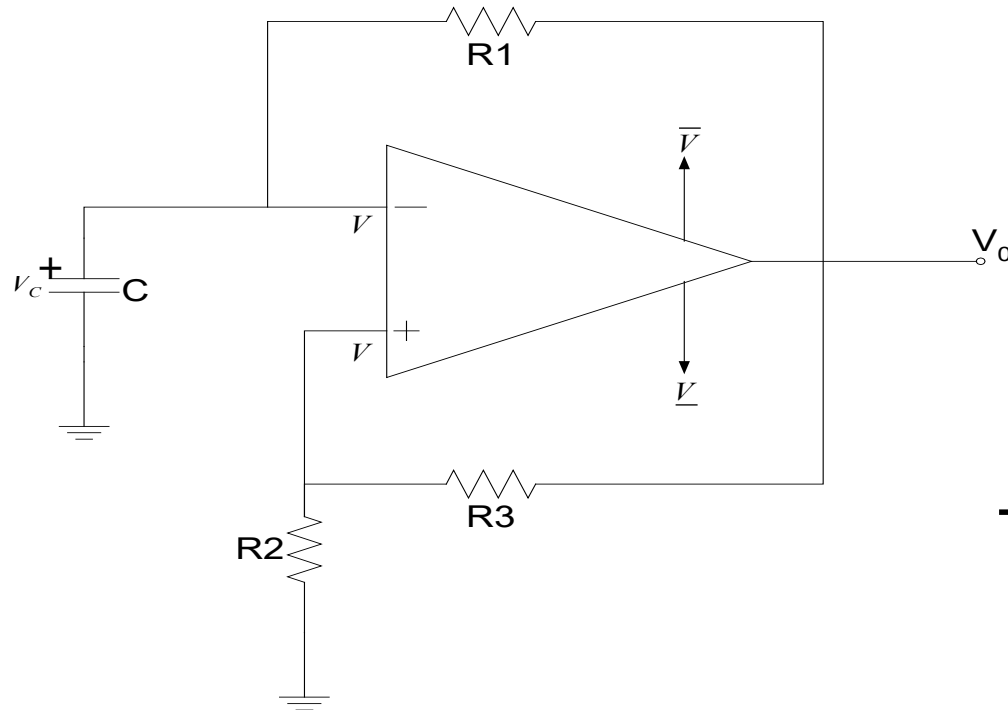- Consider a comparator with the given schematic.
 - Both positive and negative feedback
 - RC circuit that generates the inverting input V_- .




This is an **astable** multivibrator


Simple Multivibrator Output

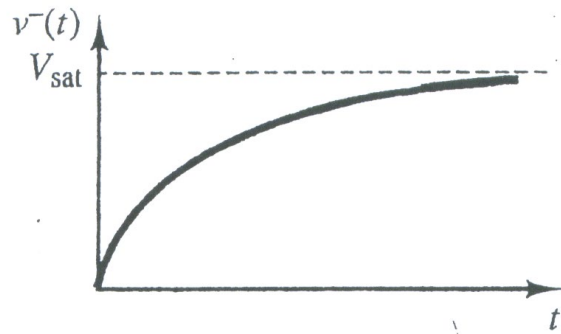


Capacitor charging

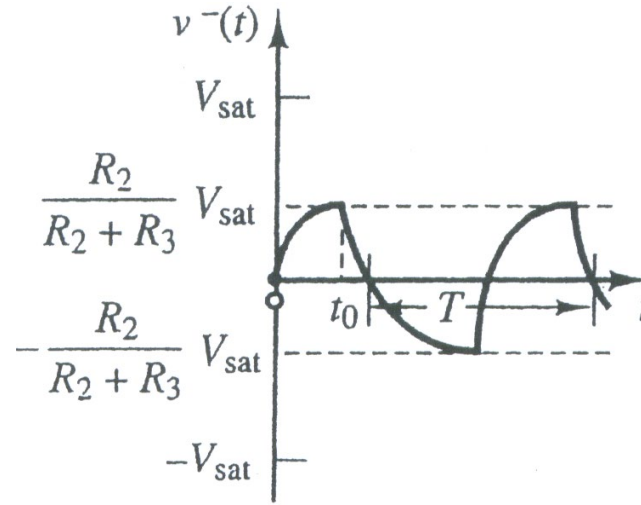

Multivibrator inverting terminal voltage

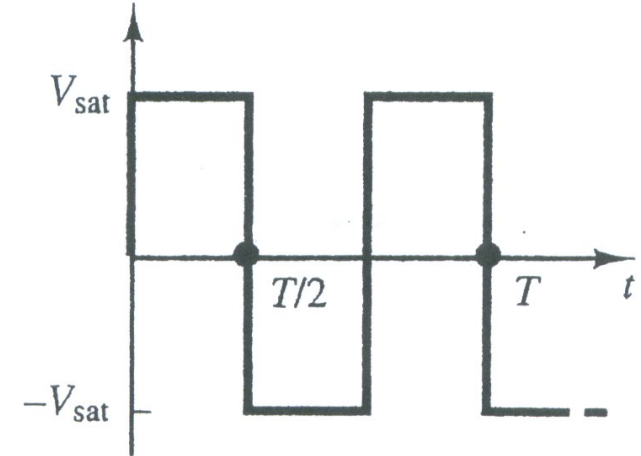

Multivibrator output waveform

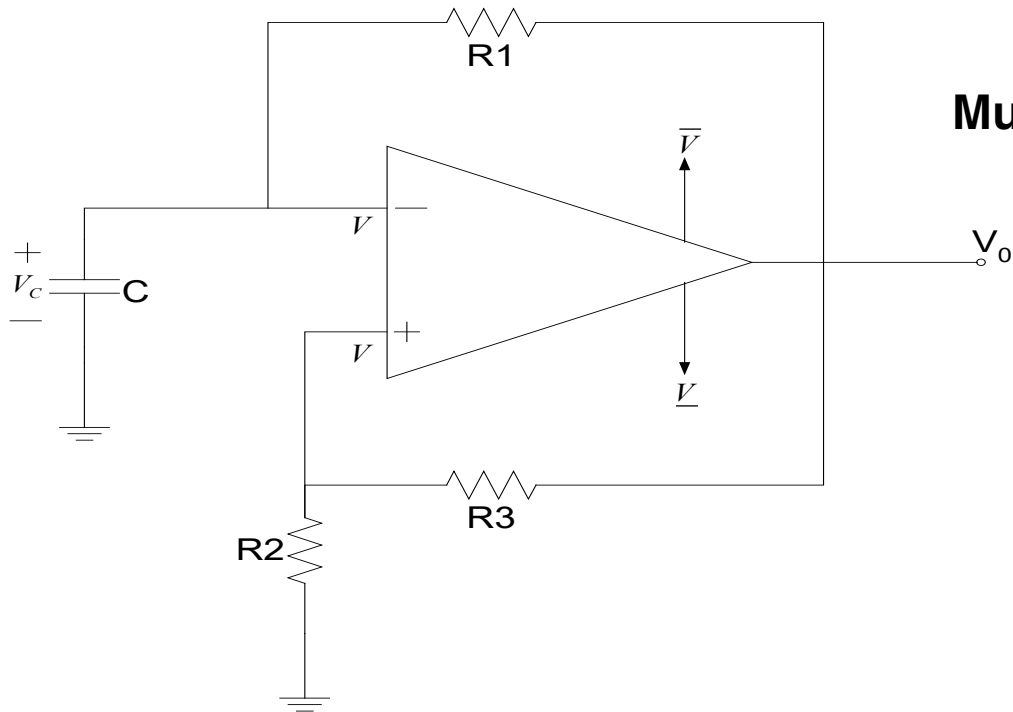

Additional Reference

- **Mathematical Details:** Topic 4 of main text details the computations for resistances and capacitances required for exact timing
- <https://www.youtube.com/watch?v=qfWljb48mjE>

Hands-on Exercises: Digital Input

BASIC Stamp Syntax and Reference Manual 2.2 RCTIME	pp. 363 – 368
What's a Microcontroller? Potentiometer (Activities #1–#3)	Chapter 5
Basic Analog and Digital 555 Timer	Chapter 6